

Name:

Date:

# CAPACITORS TEST 1

# A2-Level

Mark

Grade

# PHYSICS

---

For this paper you must have:

- Ruler
- Pencil and Rubber
- Scientific calculator, which you are expected to use when appropriate

## Instructions


- Answer all questions
- Answer questions in the space provided
- All working must be shown

## Information

- The marks for the questions are shown in brackets

1

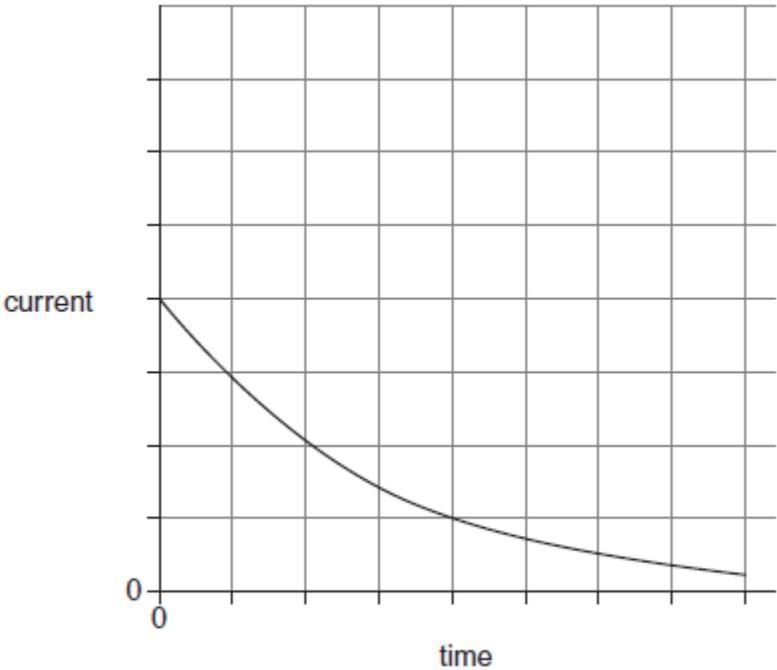(a) The graph shows how the current varies with time as a capacitor is discharged through a  $150\ \Omega$  resistor.



(i) Explain how the initial charge on the capacitor could be determined from a graph of current against time.

---

---

---

---

(1)

(ii) The same capacitor is charged to the same initial potential difference (pd) and then discharged through a  $300\ \text{k}\Omega$  resistor. Sketch a second graph on the same axes above to show how the current varies with time in this case.

(3)

- (b) In an experiment to show that a capacitor stores energy, a student charges a capacitor from a battery and then discharges it through a small electric motor. The motor is used to lift a mass vertically.
- (i) The capacitance of the capacitor is 0.12 F and it is charged to a pd of 9.0 V. The weight of the mass raised is 3.5 N. Calculate the maximum height to which the mass could be raised. Give your answer to an appropriate number of significant figures.

maximum height \_\_\_\_\_ m

(4)

- (ii) Give **two** reasons why the value you have calculated in part (i) would not be achieved in practice.

1. \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

2. \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

(2)

(Total 10 marks)

2


The specification for a pacemaker requires a suitable charge to be delivered in 1.4 ms. A designer uses a circuit with a capacitor of capacitance  $3.0 \mu\text{F}$  and a 2.5 V power supply to deliver the charge. The designer calculates that a suitable charge will be delivered to the heart as the capacitor discharges from a potential difference (pd) of 2.5 V to a pd of 1.2 V in 1.4 ms.

(a) (i) Calculate the charge on the capacitor when it is charged to a pd of 2.5 V.

charge \_\_\_\_\_ C

(1)

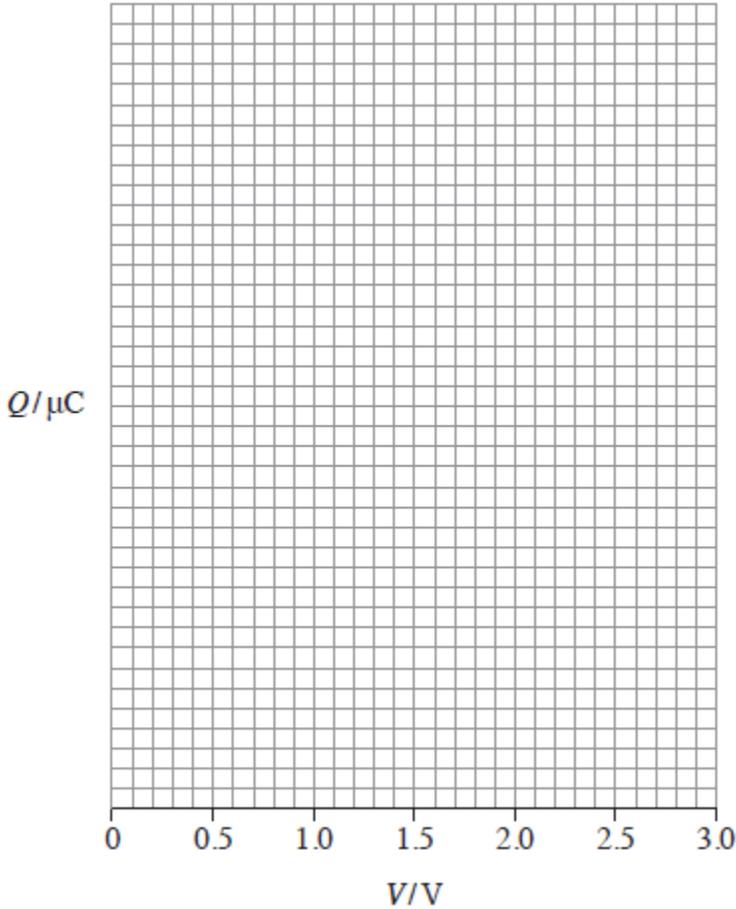(ii) Draw a graph showing how the charge,  $Q$ , on the capacitor varies with the pd,  $V$ , as it discharges through the heart.  
Include an appropriate scale on the charge axis.



(3)

- (b) Calculate the energy delivered to the heart in a single pulse from the pacemaker when the capacitor discharges to 1.2 V from 2.5 V.

energy \_\_\_\_\_ J

**(3)**

- (c) (i) Calculate the resistance of the heart that has been assumed in the design.

resistance \_\_\_\_\_  $\Omega$

**(3)**

- (ii) Explain why the rate of change of pd between the capacitor plates decreases as the capacitor discharges.

---

---

---

---

---

**(2)**

**(Total 12 marks)**

3

(a) When an uncharged capacitor is charged by a **constant** current of  $4.5 \mu\text{A}$  for  $60 \text{ s}$  the pd across it becomes  $4.4 \text{ V}$ .


(i) Calculate the capacitance of the capacitor.

capacitance \_\_\_\_\_ F

(3)

(ii) The capacitor is charged using the circuit shown in **Figure 1**. The battery emf is  $6.0 \text{ V}$  and its internal resistance is negligible. In order to keep the current constant at  $4.5 \mu\text{A}$ , the resistance of the variable resistor  $R$  is decreased steadily as the charge on the capacitor increases.

Figure 1

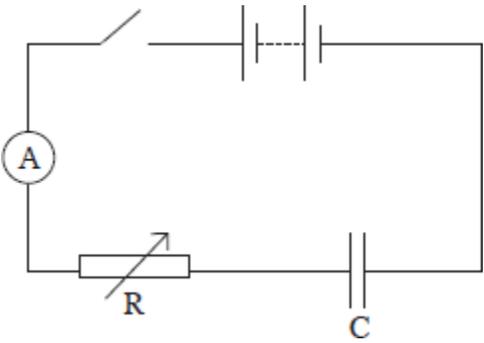

Calculate the resistance of  $R$  when the uncharged capacitor has been charging for  $30 \text{ s}$ .


resistance \_\_\_\_\_  $\Omega$

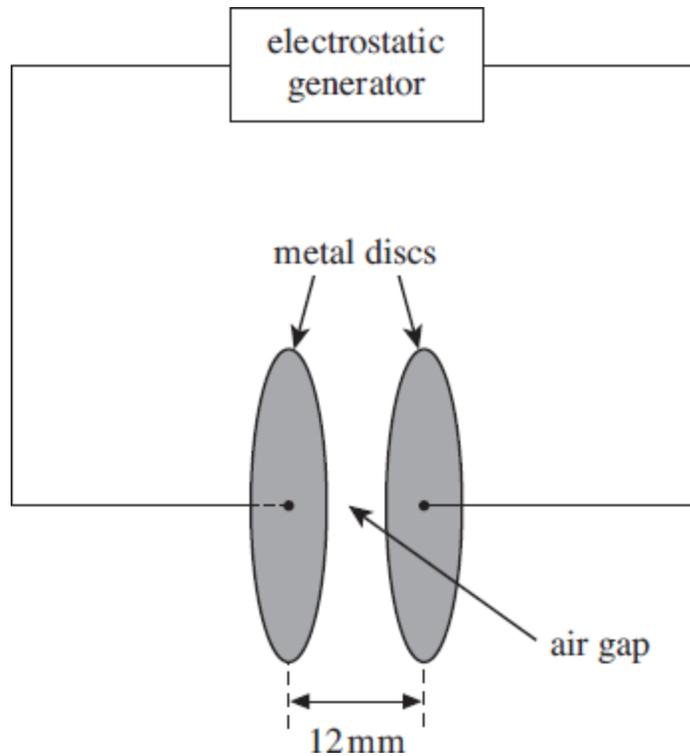(3)



4

The diagram below shows an arrangement to demonstrate sparks passing across an air gap between two parallel metal discs. Sparks occur when the electric field in the gap becomes large enough to equal the breakdown field strength of the air. The discs form a capacitor, which is charged at a constant rate by an electrostatic generator until the potential difference (pd) across the discs is large enough for a spark to pass. Sparks are then produced at regular time intervals whilst the generator is switched on.



- (a) The electrostatic generator charges the discs at a constant rate of  $3.2 \times 10^{-8}$  A on a day when the minimum breakdown field strength of the air is  $2.5 \times 10^6$  V m<sup>-1</sup>. The discs have a capacitance of  $3.7 \times 10^{-12}$  F.
- (i) The air gap is 12 mm wide. Calculate the minimum pd required across the discs for a spark to occur. Assume that the electric field in the air gap is uniform.

pd \_\_\_\_\_ V

(1)

- (ii) Calculate the time taken, from when the electrostatic generator is first switched on, for the pd across the discs to reach the value calculated in part (a)(i).

time \_\_\_\_\_ s

**(2)**

- (b) The discs are replaced by ones of larger area placed at the same separation, to give a larger capacitance.

State and explain what effect this increased capacitance will have on:

- (i) the time between consecutive discharges,

---

---

---

---

---

---

**(2)**

- (ii) the brightness of each spark.

---

---

---

---

---


---

**(2)**

**(Total 7 marks)**

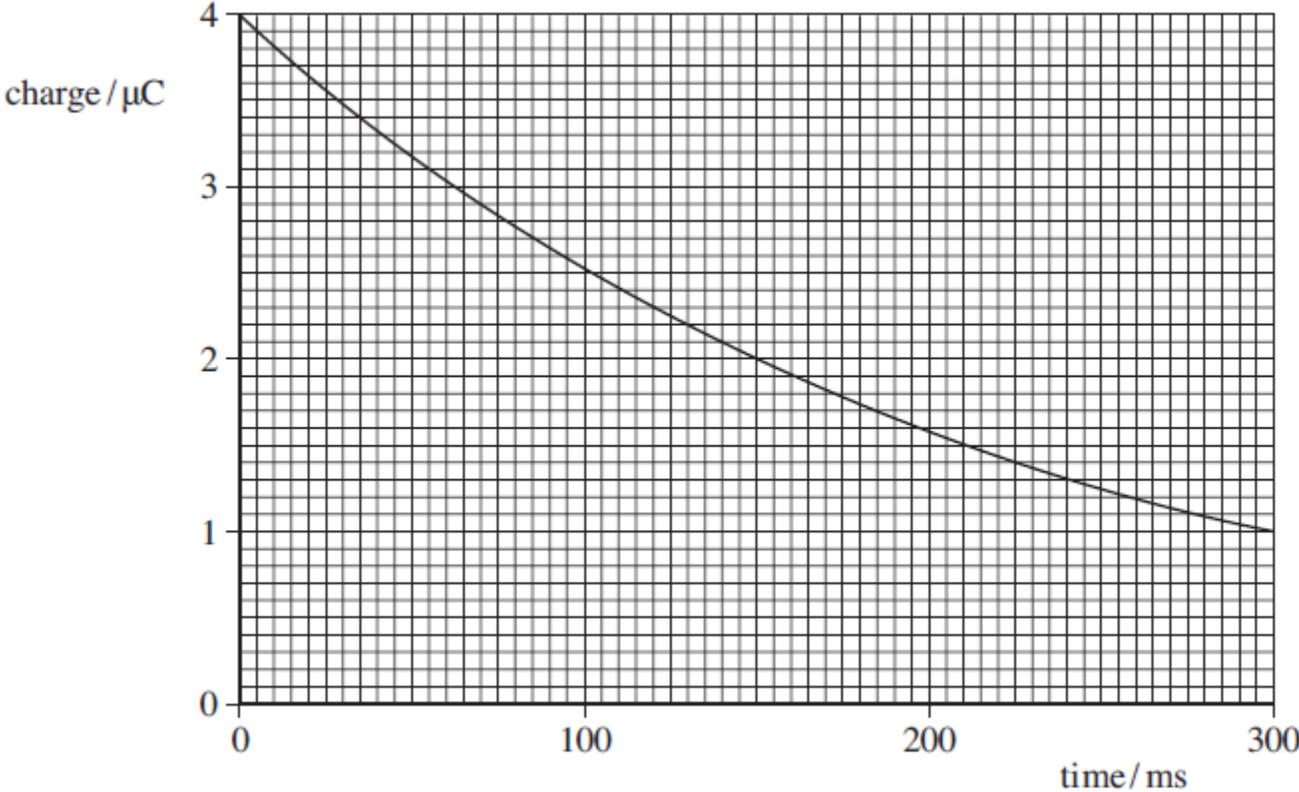**5**

The graph below shows how the charge stored by a capacitor varies with time when it is discharged through a fixed resistor.



(a) Determine the time constant, in ms, of the discharge circuit.

time constant \_\_\_\_\_ ms

**(3)**

(b) Explain why the rate of discharge will be greater if the fixed resistor has a smaller resistance.

---

---

---

---

---

**(2)**

**(Total 5 marks)**

6

(a) Define the capacitance of a capacitor.

---


---

---


---

(2)

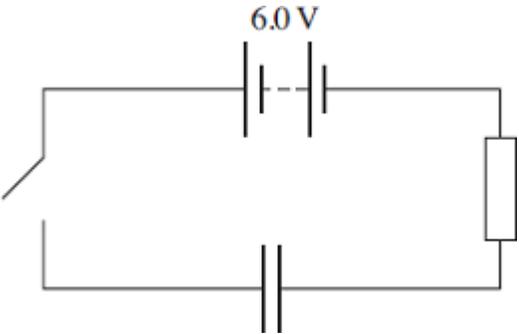(b) The circuit shown in the figure below contains a battery, a resistor, a capacitor and a switch.



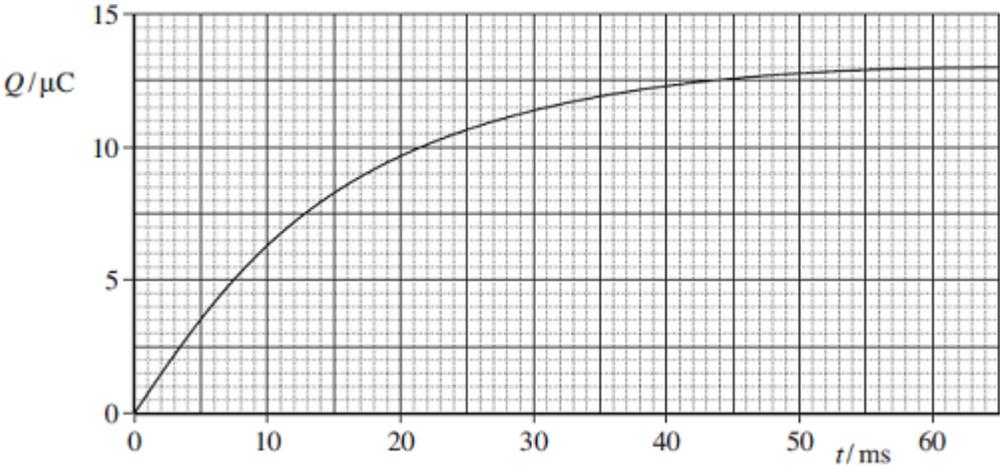The switch in the circuit is closed at time  $t = 0$ . The graph shows how the charge  $Q$  stored by the capacitor varies with  $t$ .



(b) (i) When the capacitor is fully charged, the charge stored is  $13.2 \mu\text{C}$ . The electromotive force (emf) of the battery is  $6.0 \text{ V}$ . Determine the capacitance of the capacitor.

answer = \_\_\_\_\_ F

(2)

- (ii) The time constant for this circuit is the time taken for the charge stored to increase from 0 to 63% of its final value. Use the graph to find the time constant in milliseconds.

answer = \_\_\_\_\_ ms

(2)

- (iii) Hence calculate the resistance of the resistor.

answer = \_\_\_\_\_  $\Omega$

(1)

- (iv) What physical quantity is represented by the gradient of the graph?

---

---


(1)

- (c) (i) Calculate the maximum value of the current, in mA, in this circuit during the charging process.

answer = \_\_\_\_\_ mA

(1)

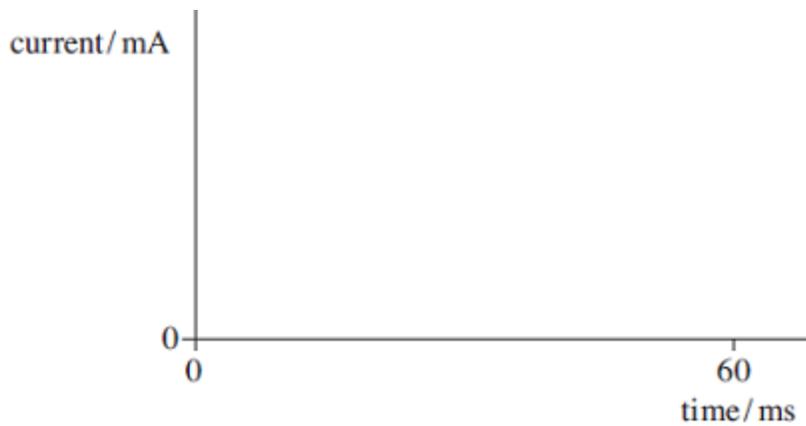- (ii) Sketch a graph on the outline axes to show how the current varies with time as the capacitor is charged. Mark the maximum value of the current on your graph.



(2)

(Total 11 marks)

7

A capacitor of capacitance  $C$  has a charge of  $Q$  stored on the plates. The potential difference between the plates is doubled.

What is the change in the energy stored by the capacitor?

A  $\frac{Q^2}{2C}$

B  $\frac{Q^2}{C}$

C  $\frac{3Q^2}{2C}$

D  $\frac{2Q^2}{C}$

(Total 1 mark)

8

A capacitor consists of two parallel square plates of side  $l$  separated by distance  $d$ . The capacitance of the arrangement is  $C$ .

What is the capacitance of a capacitor with square plates of side  $2l$  separated by a distance  $\frac{d}{2}$ ?

A  $C$

B  $2C$

C  $4C$

D  $8C$

(Total 1 mark)

9

A capacitor of capacitance  $120 \mu\text{F}$  is charged and then discharged through a  $20 \text{ k}\Omega$  resistor.

What fraction of the original charge remains on the capacitor  $4.8 \text{ s}$  after the discharge begins?

A 0.14

B 0.37

C 0.63

D 0.86

(Total 1 mark)

**10**

Initially a capacitor stores  $600 \mu\text{C}$  of charge. When it loses half of this charge, the potential difference (pd) across it decreases by  $50 \text{ V}$ .

What is the capacitance of the capacitor?

**A**     $1.5 \mu\text{F}$    

**B**     $3.0 \mu\text{F}$    

**C**     $6.0 \mu\text{F}$    

**D**     $12 \mu\text{F}$    

**(Total 1 mark)**