

Name:

Date:

# CAPACITORS TEST 3

# A2-Level

Mark

Grade

# PHYSICS

---

For this paper you must have:

- Ruler
- Pencil and Rubber
- Scientific calculator, which you are expected to use when appropriate

## Instructions

- Answer all questions
- Answer questions in the space provided
- All working must be shown

## Information

- The marks for the questions are shown in brackets

1

A  $680\ \mu\text{F}$  capacitor is charged fully from a  $12\ \text{V}$  battery. At time  $t = 0$  the capacitor begins to discharge through a resistor. When  $t = 25\ \text{s}$  the energy remaining in the capacitor is one quarter of the energy it stored at  $12\ \text{V}$ .

- (a) Determine the pd across the capacitor when  $t = 25\text{s}$ .

---

---

---

---

(2)

- (b) (i) Show that the time constant of the discharge circuit is  $36\ \text{s}$ .

---

---

---

---

---

- (ii) Calculate the resistance of the resistor.

---

---

(4)

(Total 6 marks)

**2**

(a) As a capacitor was charged from a 12 V supply, a student used a coulomb meter and a voltmeter to record the charge stored by the capacitor at a series of values of potential difference across the capacitor. The student then plotted a graph of pd (on the y-axis) against charge (on the x-axis).

(i) Sketch the graph obtained.



(ii) State what is represented by the gradient of the line.


---

(iii) State what is represented by the area enclosed by the line and the x-axis of the graph.

---

**(3)**

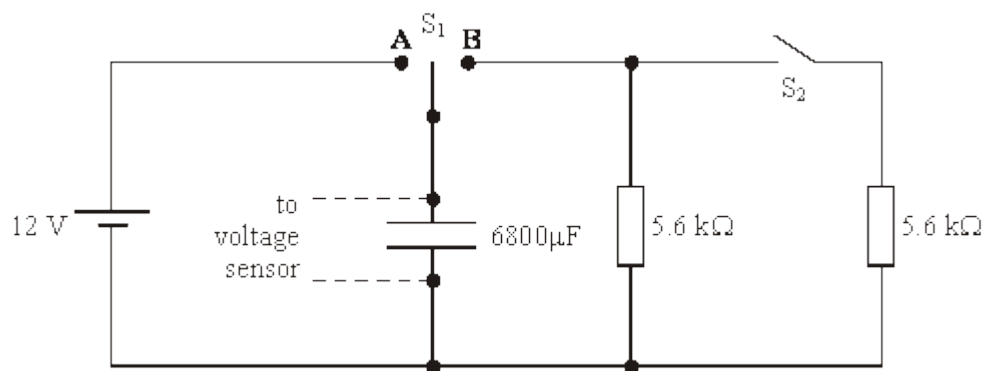- (b) The student then connected the capacitor as shown in the diagram below to carry out an investigation into the discharge of the capacitor.



The student used a voltage sensor, datalogger and computer to obtain values for the pd across the capacitor at various times during the discharge.

- (i) At time  $t = 0$ , with switch  $S_2$  open, switch  $S_1$  was moved from position **A** to position **B**. Calculate the pd across the capacitor when  $t = 26$  s.

---



---



---



---

- (ii) At time  $t = 26$  s, as the discharge continued, the student closed switch  $S_2$ . Calculate the pd across the capacitor 40 s after switch  $S_1$  was moved from position **A** to position **B**.

---



---




---



---

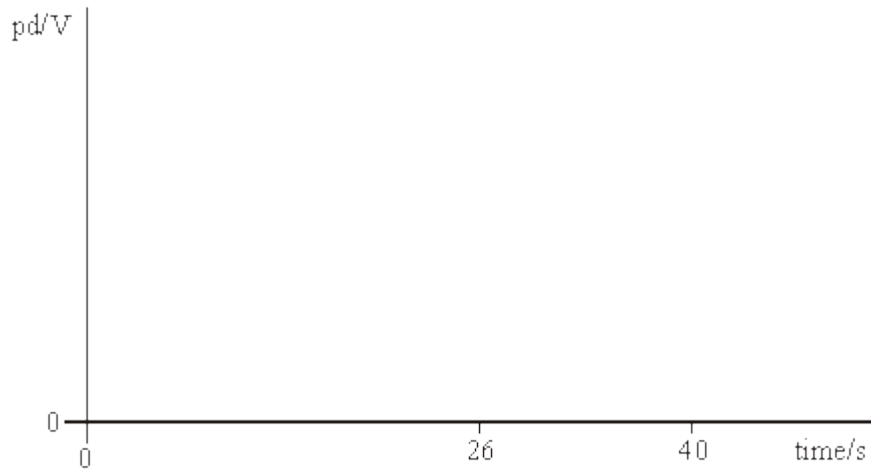- (iii) Sketch a graph of pd against time for the student's experiment described in parts (b)(i) and (b)(ii).



(7)

(Total 10 marks)

3

A capacitor of capacitance  $330 \mu\text{F}$  is charged to a potential difference of  $9.0 \text{ V}$ . It is then discharged through a resistor of resistance  $470 \text{ k}\Omega$ .

Calculate

- (a) the energy stored by the capacitor when it is fully charged,

---

---

---

---

(2)

- (b) the time constant of the discharging circuit,

---

---

(1)

(c) the p.d. across the capacitor 60 s after the discharge has begun.

---

---

---

---

---


---

(3)

(Total 6 marks)

4

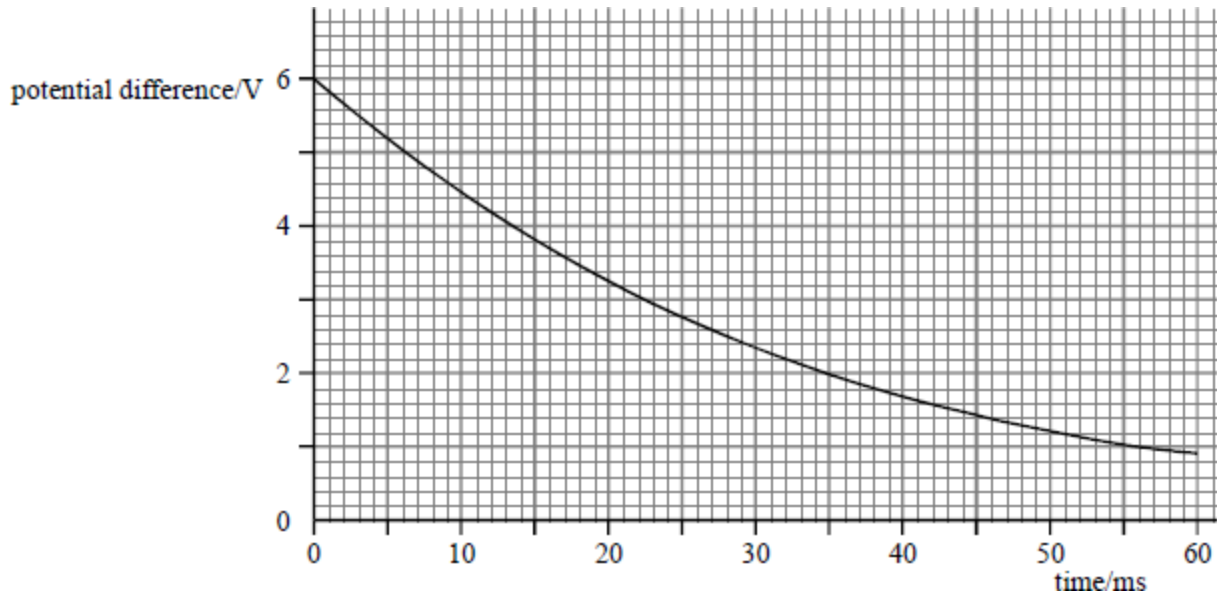A student used a voltage sensor connected to a datalogger to plot the discharge curve for a  $4.7 \mu\text{F}$  capacitor. She obtained the following graph.



Use data from the graph to calculate

(a) the initial charge stored,

---

(2)

(b) the energy stored when the capacitor had been discharging for 35 ms,

---

---

(3)

(c) the time constant for the circuit,

---

---

---

---

(3)

(d) the resistance of the circuit through which the capacitor was discharging.

---

---


---

(2)

(Total 10 marks)

5

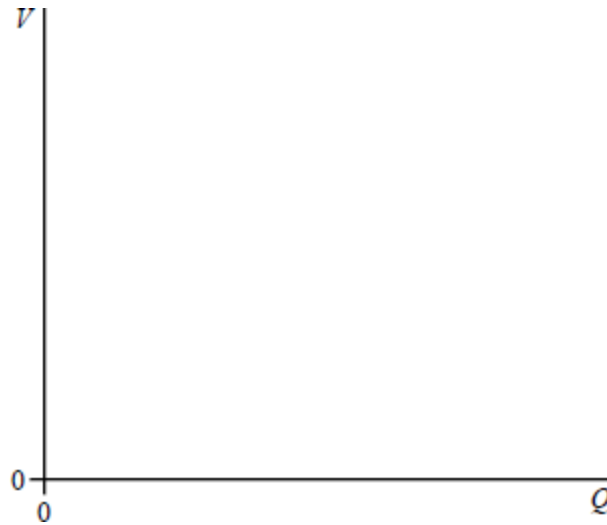(a) A  $2.0 \mu\text{F}$  capacitor is charged through a resistor from a battery of emf  $4.5 \text{ V}$ . Sketch a graph on the axes below to show how the charge stored,  $Q$ , varies with the potential difference,  $V$ , across the capacitor during the charging process. Mark appropriate values on the axes of the graph.



(2)

- (b) (i) Show that the energy stored by a charged capacitor is given by  $E = \frac{1}{2}QV$ .

---

---

---

---

---

---

---

- (ii) Calculate the energy stored by the capacitor in part (a) when the potential difference across it is 1.5 V.

---

---

---

---


---

(5)

(Total 7 marks)

6

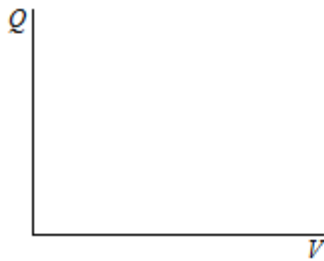- (a) For a capacitor of capacitance  $C$ , sketch graphs of charge,  $Q$ , and energy stored,  $E$ , against potential difference,  $V$ .



graph A



graph b

What is represented by the slope of graph A?

---

(3)



(b) A capacitor of capacitance 0.68 F is charged to 6.0 V. Calculate

(i) the charge stored by the capacitor,

---

---

(ii) the energy stored by the capacitor.

---

---

(2)

(Total 5 marks)

**7** An initially uncharged capacitor of capacitance 20  $\mu\text{F}$  is charged by a constant current of 80  $\mu\text{A}$ . Which line, **A** to **D**, in the table gives the potential difference across, and the energy stored in, the capacitor after 50 s?

|          | potential difference / V | energy stored / J    |
|----------|--------------------------|----------------------|
| <b>A</b> | $4.0 \times 10^{-3}$     | $2.0 \times 10^{-3}$ |
| <b>B</b> | $4.0 \times 10^{-3}$     | $4.0 \times 10^{-1}$ |
| <b>C</b> | $2.0 \times 10^2$        | $2.0 \times 10^{-3}$ |
| <b>D</b> | $2.0 \times 10^2$        | $4.0 \times 10^{-1}$ |

(Total 1 mark)

**8** Which one of the following statements about a parallel plate capacitor is **incorrect**?

- A** The capacitance of the capacitor is the amount of charge stored by the capacitor when the pd across the plates is 1V.
- B** A uniform electric field exists between the plates of the capacitor.
- C** The charge stored on the capacitor is inversely proportional to the pd across the plates.
- D** The energy stored when the capacitor is fully charged is proportional to the square of the pd across the plates.

(Total 1 mark)

**9**

A  $1000\ \mu\text{F}$  capacitor and a  $10\ \mu\text{F}$  capacitor are charged so that they store the same energy. The pd across the  $1000\ \mu\text{F}$  capacitor is  $V_1$  and the pd across the other capacitor is  $V_2$ .

What is the value of the ratio  $\left(\frac{V_1}{V_2}\right)^2$ ?

**A**  $\frac{1}{1000}$

**B**  $\frac{1}{100}$


**C**  $\frac{1}{10}$

**D** 10

(Total 1 mark)

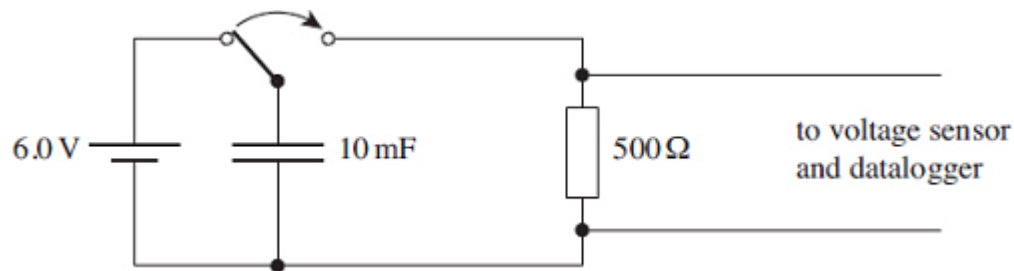**10**

A voltage sensor and a datalogger are used to record the discharge of a  $10\ \text{mF}$  capacitor in series with a  $500\ \Omega$  resistor from an initial pd of  $6.0\ \text{V}$ . The datalogger is capable of recording 1000 readings in  $10\ \text{s}$ . Which line, **A** to **D**, in the table gives the pd and the number of readings made after a time equal to the time constant of the discharge circuit?



|          | potential difference/V | number of readings |
|----------|------------------------|--------------------|
| <b>A</b> | 2.2                    | 50                 |
| <b>B</b> | 3.8                    | 50                 |
| <b>C</b> | 3.8                    | 500                |
| <b>D</b> | 2.2                    | 500                |

(Total 1 mark)